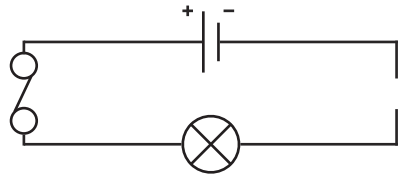
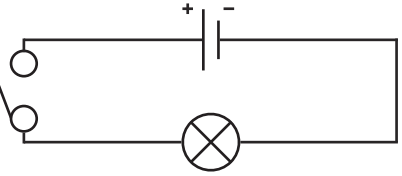
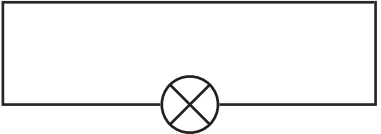
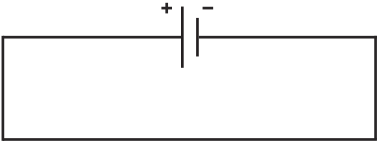
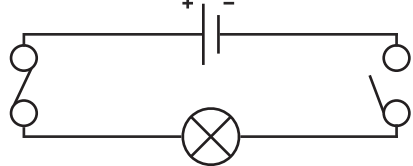


# Find the Problem With the Electrical Circuit

Fault Finding Circuit Number	Will the bulb light? yes/no	Where is the fault on the circuit? Circle the fault.	Draw the correct circuit that will light the bulb.	Describe how you fixed the fault to light the bulb.
1				
2				
3				
4				
5				
6		